



Reg. No.

--	--	--	--	--	--	--	--	--	--

**BSCPHC 281**

**Choice Based Credit System IV Semester B.Sc. Examination, September 2022  
(2020-21 Batch Onwards)  
PHYSICS  
Electricity and X-ray Crystallography**

Time : 3 Hours

Max. Marks : 80

- Instructions :** 1) Answer questions from **all** Units.  
2) Scientific calculators are **allowed**.

**PART – A**

1. Answer **any eight** of the following : **(1×8=8)**
- What is the internal resistance of an ideal current source ?
  - What are transient currents ?
  - State superposition theorem.
  - What is wattless current ?
  - What is band pass filter ?
  - Define magnetic flux density.
  - What is damping in B.G ?
  - What are Miller Indices ?
  - State Bragg's law.
2. Answer **any six** of the following : **(2×6=12)**
- Show that  $L/R$  has dimension of time.
  - State Kirchhoff's laws.
  - Why a series LCR circuit called an acceptor circuit ?
  - Distinguish between Inductive reactance and Capacitive reactance.
  - What is magnetic dipole and magnetic dipole moment ?
  - Define charge sensitivity of a B.G and write its unit.
  - State and explain Mosley's law.
  - Explain isotopic effect in a super conductor.

**P.T.O.**



## PART – B

## Unit – I


3. a) Derive an expression for the growth of charge in a CR circuit. 4  
 b) State Norton's theorem. Explain the method of Nortonising the circuit. Explain how Thevenin's equivalent can be obtained from Norton's equivalent. 7

OR

4. a) State and prove maximum power transfer theorem. 4  
 b) Give the theory of discharging of a capacitor in LCR circuit. 7
5. a) A battery of emf 100 V is connected in series with an inductance of 100 mH and a capacitor of  $0.05 \mu\text{F}$  and a resistor of  $100 \Omega$ . Find :  
 i) The frequency of the oscillatory current  
 ii) The final charge on the capacitor. 4

OR

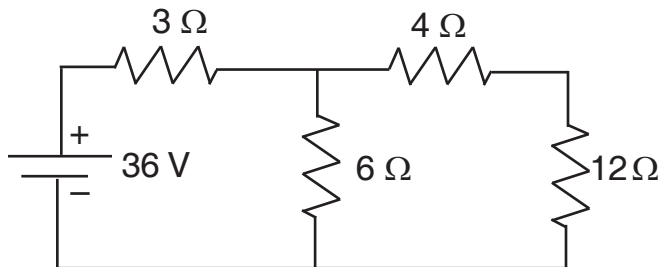- b) Apply Thevenin's theorem to find the current through  $12 \Omega$  resistor of the circuit. 4



## Unit – II

6. a) Obtain the relationship between rms value and peak value of current. 4  
 b) Derive an expression for the current in a series LCR circuit. Hence obtain the expression for resonance frequency. 7

OR

7. a) Derive an expression for Power in an AC circuit. 4  
 b) Discuss about RC Low pass filter and derive an expression for cut-off frequency. 7



8. a) An AC circuit consists of a coil of resistance  $15 \Omega$  and inductive reactance  $20 \Omega$  and is worked at 200 V, 50 Hz supply. Find the value of current and phase lag. **4**

OR

- b) A circuit contains capacitor of  $50 \mu\text{F}$ , an inductance of 5 H and a resistor of  $15 \Omega$  all in series with a 220 V, 50 Hz AC supply. Calculate the resonant frequency and Q-factor of a series LCR circuit. **4**

**Unit – III**

9. a) Obtain the formula for the force on a current carrying conductor placed in a magnetic field. **4**  
b) Give the theory of B.G and obtain an expression for the charge passing through it. **7**

OR

10. a) Give the theory of De-Sauty bridge to find the ratio of capacitances. **4**  
b) Give the theory of Anderson's bridge. **7**

11. a) A condenser is charged to a potential of 2 V and then discharged through a B.G giving a throw of 10 cm. If its period is 7.2s and the current sensitivity is  $\frac{1}{30} \mu\text{A/cm}$ . Calculate the capacitance of the condenser. **4**

OR

- b) A circular coil of area  $5 \text{ cm}^2$  and having 100 turns is placed in a uniform magnetic field of 1.5 T. When a current of 0.2 A is passed through the coil, find the magnetic dipole moment of the coil and maximum torque produced. **4**

**Unit – IV**

12. a) Explain the origin of characteristic X-rays. **4**  
b) What is superconductivity and transition temperature ? Explain Meissner effect and the action of external magnetic field on a superconductor. **7**

OR



13. a) Explain two applications of superconductor. **4**
- b) Describe Bragg's Spectrometer and explain how it is used to determine the wavelength of X-rays. **7**
14. a) Monochromatic X-ray beam of wavelength  $0.7\text{\AA}$  undergo first order Bragg's reflection from the plane (302) of a cubic crystal at a glancing angle of  $39^{\circ}7'19''$ . Calculate the lattice constant. **4**

OR

- b) First order Bragg's reflection occurs when monochromatic beam of X-rays of wavelength  $0.675\text{\AA}$  is incident on a crystal at a glancing angle of  $4^{\circ}51'$ . What is the glancing angle for third order Bragg reflection to occur? **4**
-